



COLLEGE OF ENGINEERING, DESIGN, ART &  
TECHNOLOGY

SCHOOL OF ENGINEERING

DEPARTMENT OF ELECTRICAL & COMPUTER  
ENGINEERING

## Assignment 1

### Transmission Lines

Submitted by

**Kakooza Abraham Jerry**

16/U/327

216000136


### Group Members

Name	Reg. No.
Kakooza Abraham Jerry	16/U/327
Mbarebaki Adonai	16/U/
Peter Claver	16/U/
Akhol Peter	16/U/

19<sup>th</sup> October, 2020

## Solution to Question 1

- Given the figure below

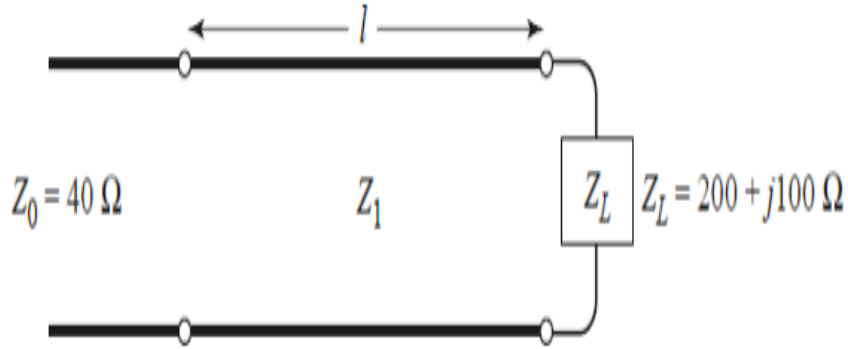

$$Z_{\text{in}} = Z_0 = 40 \Omega$$

$$Z_{\text{in}} = Z_1 \left( \frac{Z_L + jZ_1 \tan \beta l}{Z_1 + jZ_L \tan \beta l} \right),$$

let  $t = \tan \beta l$  such that

$$Z_{\text{in}} = Z_1 \left( \frac{(200 + j100) + jZ_1 t}{Z_1 + j(200 + j100)t} \right),$$

$$(40Z_1 - 4000t) + j8000t = 200Z_1 + j(100 + Z_1 t)Z_1$$

Equating real and imaginary factors

Re:

$$40Z_1 - 4000t = 200Z_1$$

$$160Z_1 = -4000t$$

$$Z_1 = -25t$$

Im:

$$5000t = Z_1(100 + Z_1 t)$$

$$8000t = -25t(100 - 25t)$$

$$000t = -2500t + 625t^3$$

$$t(625t^2 - 10500) = 0$$

Either  $t = 0$

Or

$$(625t^2 - 10500) = 0$$

$$t = \pm\sqrt{16.8}$$

$$t = \pm 4.1$$

Therefore  $t = -4.1$ , so that  $Z_1 = 102.5\Omega$

From  $t = \tan \beta l$

$$\beta l = \arctan t = \arctan -4.1 = -76.3^\circ \Leftrightarrow 104^\circ$$


$\therefore$

$$\frac{2\pi l}{\lambda} = 104$$


$$l = 0.289\lambda$$

## Solution to Question 2

2. Given the figure below

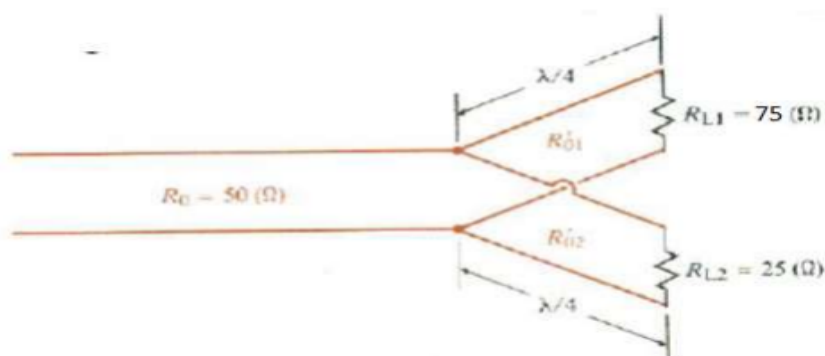

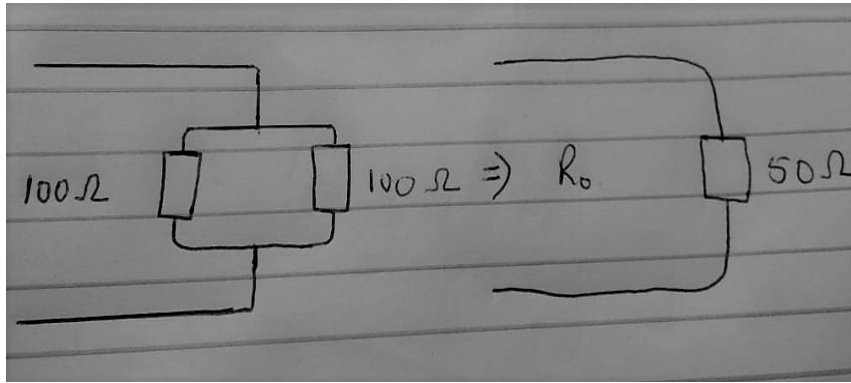- (a) The input impedance of the two branch looking at the junction from the  $50\Omega$  line must be equal to  $100\Omega$  such that when they are in parallel the resultant impedance is  $50\Omega$



$$Z_{in_1} = R_{in_1} = 100\Omega$$

The characteristics impedance

$$R_{o1} = \sqrt{R_{in_1} R_{L_1}} = \sqrt{100 \times 75} = 86.6\Omega$$

Similarly

$$R_{o2} = \sqrt{R_{in_2} R_{L_2}} = \sqrt{100 \times 25} = 50\Omega$$

Physical length,  $l_P = 0.5c$

From

$$\frac{1}{\sqrt{\mu_o \epsilon}} = 0.5c$$

$$\frac{1}{\sqrt{\mu_o \epsilon_o \epsilon_r}} = 0.5c$$

$$\begin{aligned} \epsilon_r &= \frac{4}{\mu \epsilon_r c^2} \\ &= \frac{4}{8.85 \times 10^{-12} \times 1.26 \times 10^{-6} \times (3 \times 10^8)^2} \end{aligned}$$

$$\epsilon_r = 4$$

Wavelength along the transformers

$$\begin{aligned}
\lambda &= \frac{0.5c}{f} \\
&= \frac{0.5 \times 3 \times 10^8}{100 \times 10^6} \\
&= 1.5m
\end{aligned}$$

Physical length of the transformers

$$\frac{\lambda}{4} = \frac{1.5}{4} = 0.375m$$

(b) When matched,  $SWR = 1$ , on the main transmission line

$$\begin{aligned}
\Gamma_{L_1} &= \frac{R_{L_1} - R_{o_1}}{R_{L_1} + R_{o_1}} \\
&= \frac{75 - 86.6}{75 + 86.6} = -0.072
\end{aligned}$$

$$\begin{aligned}
SWR_1 &= \frac{1 + |\Gamma_{L_1}|}{1 - |\Gamma_{L_1}|} \\
&= \frac{1 + 0.072}{1 - 0.072} = 1.16
\end{aligned}$$

Similarly

$$\begin{aligned}
\Gamma_{L_2} &= \frac{R_{L_2} - R_{o_1}}{R_{L_2} + R_{o_1}} \\
&= \frac{25 - 50}{25 + 50} = -0.33
\end{aligned}$$

$$\begin{aligned}
SWR_2 &= \frac{1 + |\Gamma_{L_2}|}{1 - |\Gamma_{L_2}|} \\
&= \frac{1 + 0.33}{1 - 0.33} = 1.99
\end{aligned}$$