



COLLEGE OF ENGINEERING, DESIGN, ART &
TECHNOLOGY

SCHOOL OF ENGINEERING

DEPARTMENT OF ELECTRICAL & COMPUTER
ENGINEERING

Assignment 1

Smith Charts

Submitted by

Patrick Odong

16/U/1012

216000495

Group Members

Name	Reg. No.
Odong Patrick	16/U/1012
Kirabo Doreen Zawedde	16/U/6074/PS
Gore Richard	16/U/4845/PSA
Iradukunda Silvan	16/U/4938/PS

19th October, 2020

Solution

1.

$$Z_L = 20 + j50\Omega$$

$$\bar{Z}_L = \frac{20 + j50}{50}$$

$$\bar{Z}_L = 0.4 + j1$$

(i)

$$\text{SWR} = 5.2$$

(ii) Given that $l = 0.3\lambda$, we move towards the generator $(0.135 + 0.3)\lambda = 0.435\lambda$ position

$$Y_{in} = 0.75 + j1.2$$

\therefore

$$Y_{in} = \frac{0.75 + j1.2}{50}$$

$$Y_{in} = 0.015 + j0.024S$$

(iii) $l_{min} = 0.365\lambda$ (from open circuit towards the load) $l_{max} = 0.25\lambda - 0.135\lambda = 0.115\lambda$
(from ∞ towards the load)